

Lab 2 Evaluation Sheet

Section: _____
 Student Name: _____
 Mg: _____

Prelab Exercises	TA Initials	Score
Complete VHDL code for the design	_____	_____/05
Adequate commenting of the ALU VHDL code	_____	_____/05
Student test bench for ALU	_____	_____/05
Simulation results demonstrating correct operations of ALU using student test bench	_____	_____/05
Successful clean net list synthesis	_____	_____/02
Lab Exercises		
Hardware verification		
(4) NOR, OR, AND, XOR		
(2) SL		
(2) SR		
(2) ADD		
(2) SUB	_____	_____/12
TA Grading Script		
Successful simulation of ALU source using submitted design and TA test bench	_____	_____/32
Draw a schematic of the internal logic of the barrel shifter. (Hint: it can be done with 5 muxes and 5 static shifters)	_____	_____/02